

Educational hardware trainer for teaching the Dual Active Bridge in a DC Grid.

THUAS Delft, The Netherlands

S.J.C. Koning(presenter), D.C. Zuidervliet, P.J. van Duijsen(presenter)




dc-lab.org

June 11-13 , 2024


- 1 Introduction
- 2 Overview
- 3 Topology
- 4 Modulation
- 5 Simulation
- 6 Hardware Trainer
- 7 Measurements
- 8 Conclusions

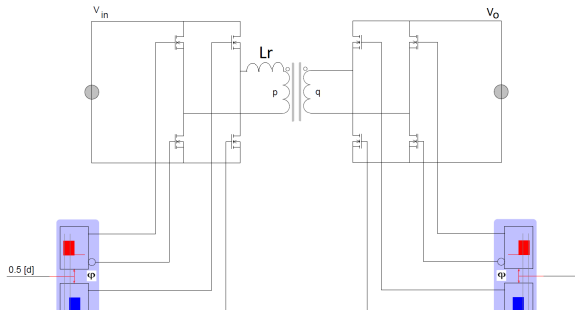Task: Teaching the application of the Dual Active Bridge using a Hardware Trainer

- Dual Active Bridge [DAB]
- Topology and Modulation
- Design and Simulation
- Hardware Trainer



Dual Active Bridge

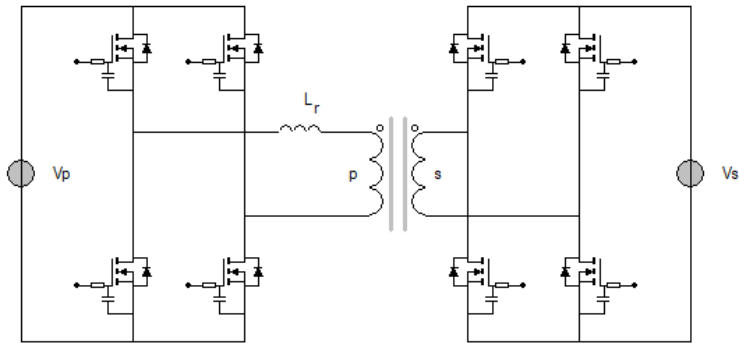

Dual Active Bridge with leakage inductance shown next to the coupled inductors.

CaspoE

Home Tools Help

Dual Active Bridge

Input and output

Input voltage Vin [V]

Output voltage Vout [V]

Control

Switching Frequency Fs [kHz]

Duty cycle primary side dp [0.0.5]

Duty cycle secondary side ds [0.0.5]


Phase shift phi [0.360Degrees]

Parameter


Leakage inductor value L [μ H]

Calculate

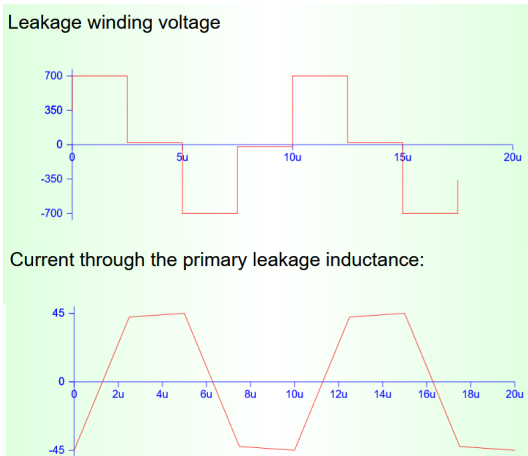Design tool to calculate the current waveform and power transfer.



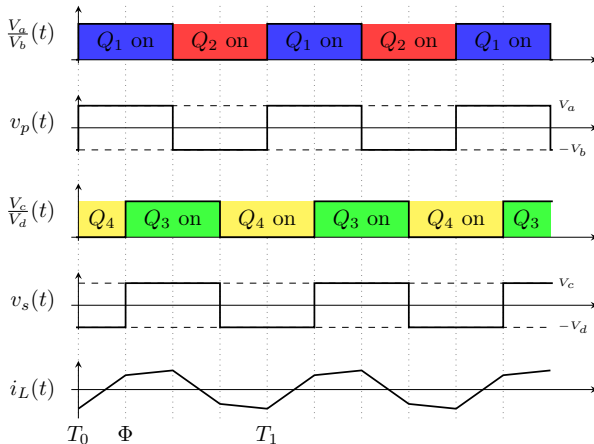Voltage across and current through the leakage inductor L_r .



Phase-shift modulation, showing the Mosfet state, Bridge voltages and current through the leakage inductor L_r .

$$P_{Nom} \propto \frac{V_{max}^2}{F_s \cdot L_{Leakage}} \quad (1)$$

$$i_0 = \frac{T_s}{2L_r} \left(-\frac{V_{in}}{2} + \frac{nV_o}{2} - nV_o \frac{\varphi}{\pi} \right) \quad (2)$$

$$i_\varphi = \frac{T_s}{2L_r} \left(-\frac{V_{in}}{2} + \frac{nV_o}{2} + V_{in} \frac{\varphi}{\pi} \right) \quad (3)$$


$$i_\pi = \frac{T_s}{2L_r} \left(\frac{V_{in}}{2} - \frac{nV_o}{2} + nV_o \frac{\varphi}{\pi} \right) \quad (4)$$

$$P_o = \frac{nV_{in}V_o}{2f_s L_r} \frac{\varphi}{\pi} \left(1 - \frac{\varphi}{\pi} \right) \quad (5)$$

$P_{in}=7.65[kW]$ $T_{p2}=5[\mu s]$ $T_{p3}=5[\mu s]$ $T_{p4}=10[\mu s]$ $T_{s1}=2.5[\mu s]$ $T_{s2}=2.5[\mu s]$
 $T_{s3}=7.5[\mu s]$ $T_{s4}=7.5[\mu s]$ $T_{s5}=10[\mu s]$


$t=$	$0\mu s$	$0\mu s$	$2.5\mu s$	$2.501\mu s$	$5\mu s$	$5.001\mu s$	$7.5\mu s$	$7.501\mu s$	$10\mu s$	$10\mu s$
$V_L=$	340V	700V	360V	20V	-340V	-700V	-360V	-20V	340V	340V
$I_L=$	-44.991A	-44.983A	42.483A	42.501A	45A	44.983A	-42.483A	-42.501A	-45A	-44.991A
$I_{in}=$	0A	-44.983A	42.483A	42.501A	45A	-44.983A	42.483A	42.501A	45A	0A

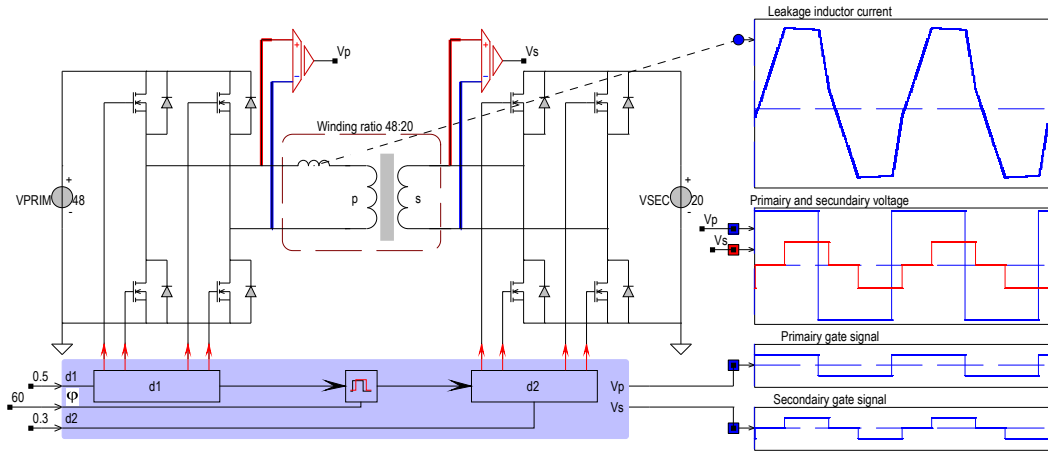Calculated current maxima and power transfer.




Simulation in Caspoc, of a DAB using two full bridges. The scope show from top to bottom, leakage inductor current, primary and secondary transformer voltages and left and right bridge gate signal.


Simplified Simulation Model

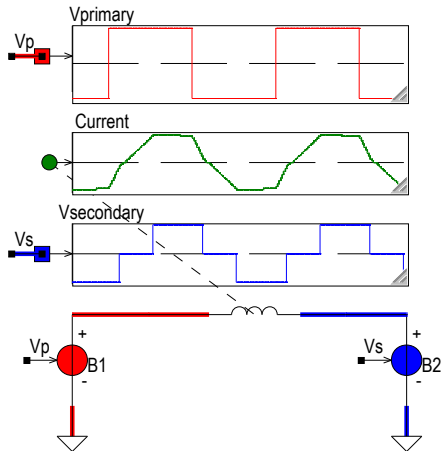

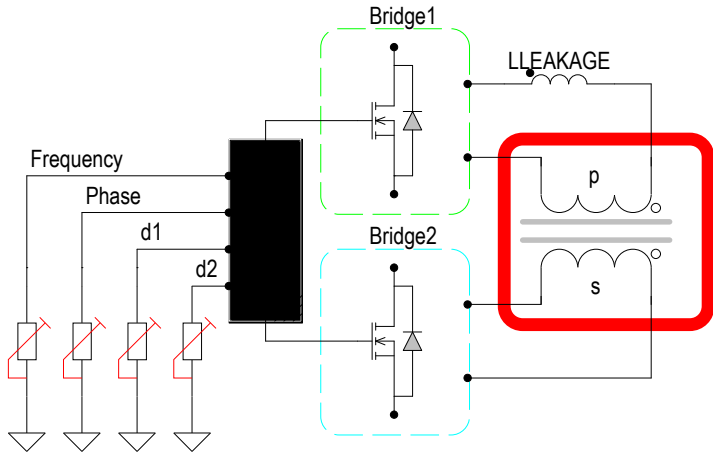
Simplified model in Caspoc, containing the two bridge voltages as controlled voltage sources coupled by only the leakage inductor L_r .



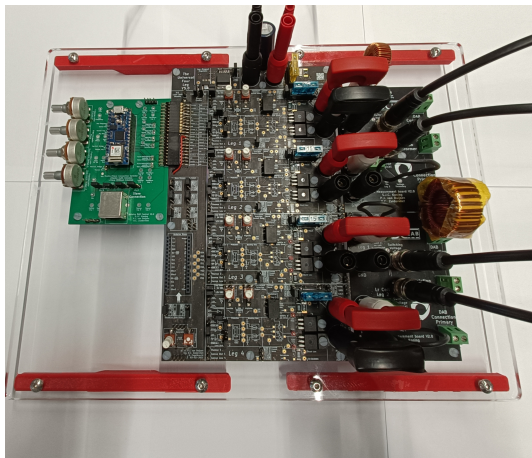
Principle schematic of the low voltage hardware trainer for the DAB, with manual controls for frequency, phase-shift and duty-cycles.



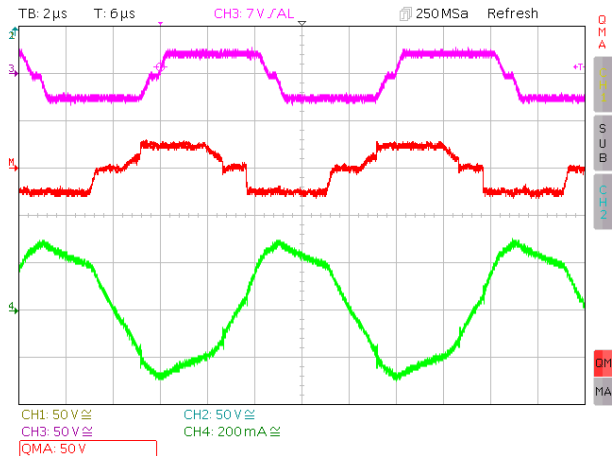Low voltage hardware trainer, where switching frequency, duty cycles and phase shift can be manually changed by the student during operation of the DAB. Voltages across and current through the transformer can be measured with the coaxial cables.



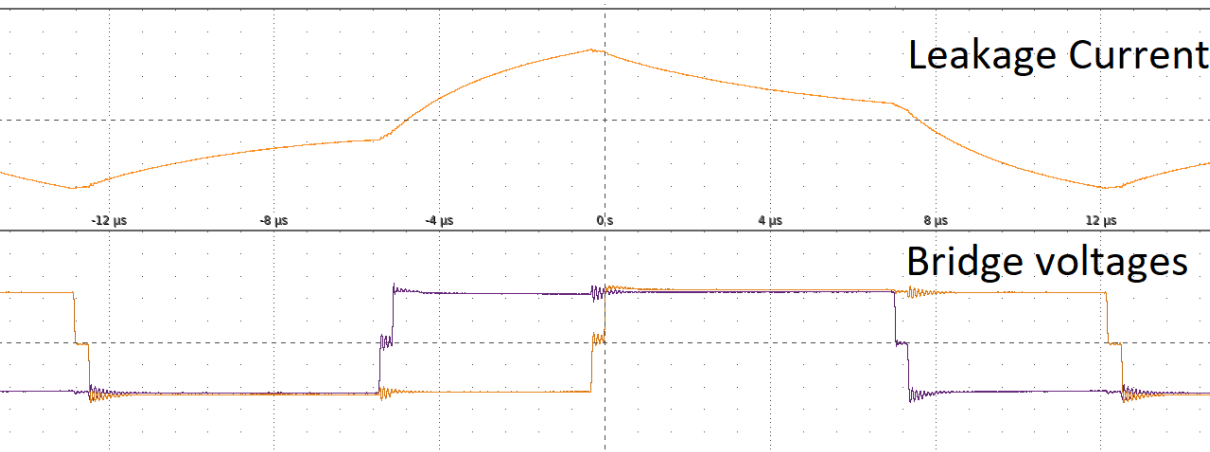Lower trace, leakage inductor current ($I_{pp}=1.0$ Ampere), and bridge output voltages ($V_{pp}=48v$), of the DAB with phase difference of 45 degrees, operating at 100kHz, $V_{dc}=24v$.



Measurement of full power transfer for $\varphi = 75^\circ$. From top to bottom: Leakage inductor current [Ch5-Orange, 5A/div, 4 $\mu\text{s}/\text{div}$] and primary [Math1-Orange] and secondary [Math2-Purple] transformer voltage [50V/div, 4 $\mu\text{s}/\text{div}$].

- Dual Active Bridge functionality
- Modulation
- Design tools and Simulation
- Hardware Trainer

Thank you!

<https://www.dc-lab.org>

P.J.vanDuijsen@hhs.nl

